
Nama : Yusuf Ade Putra Perdana

NIM : L200180169

Kelas : F

Nomor 1

A.

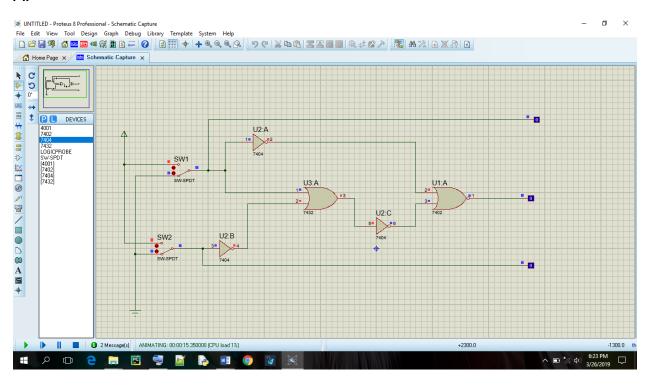

B.Fungsi bolean $(Y+X) + \overline{X} = (Y+\overline{X}) + X$

C. Tabel kebeneran

X	Υ	L1	L2	Z
0	0	0	0	0
1	0	1	0	1
0	1	0	1	0
1	1	1	1	1

Diagram Waktu

X				
	0	1	0	1
Υ				
	0	0	1	1
Z				
	0	1	0	1

Nomor 2

